

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3302**Roll No.**

--	--	--	--	--	--	--	--	--	--

B.Tech.**(SEM. II) EVEN THEORY EXAMINATION 2012-13****ELECTRONICS ENGINEERING***Time : 3 Hours**Total Marks : 100***Note :- All Sections are compulsory.****SECTION-A**

1. All parts are compulsory. Write short answers by giving proper reasons : (2×10=20)
 - (a) Find the value of DC resistance of a Germanium Junction diode at 25°C with $I_0 = 25 \mu\text{A}$ and an applied voltage of 0.2 V across the diode.
 - (b) Differentiate between Transition capacitance (C_T) and Diffusion capacitance (C_D) of a PN junction diode.
 - (c) Draw a neat diagram of a full wave rectifier bridge circuit using Diode.
 - (d) Write an expression for the ripple factor and efficiency for half wave rectifier.
 - (e) The BJT has $I_E = 10 \text{ mA}$ and $a = 0.98$. Determine the values of I_B and β .
 - (f) Sketch the input and output characteristic curve of Common Base (CB) BJT configuration.
 - (g) A FET has a drain current of 4 mA if $I_{DSS} = 8 \text{ mA}$, $V_{GS(OFF)} = -6 \text{ V}$. Find the value of V_{GS} and Pinch off voltage (V_P).
 - (h) Enlist the characteristics of an Ideal Op-Amp.
 - (i) Realize the logic expression $F = A + B\overline{C\overline{D}}$ using NAND gate only.

- (j) Convert the $(6089.25)_{10} \rightarrow ()_8$.

SECTION-B

2. Attempt any **three** parts of the following : $(10 \times 3 = 30)$

- (a) Draw a neat diagram of Zener voltage regulator circuit and determine the load resistance (R_L) and range of series resistance (R) value to meet the following specification : Output Voltage (V_{out}) = 5 V, Load Current (I_L) = 10 mA, Zener maximum wattage = 400 mW and Input Voltage (V_{in}) = 10 ± 2 V.
- (b) Draw a neat diagram and explain the working of a Center tap type full wave rectifier. Calculate the value of capacitance to use as a shunt capacitor filter in full wave rectifier with the given specification : Operating frequency 50 Hz, ripple factor 10% and load resistance is 1 k Ω .
- (c) For voltage divider common source JFET configuration as shown in Figure 1, if $V_D = 12$ V and $V_{GSQ} = -2$ V, determine the value of resistance (R_S) :

 


Figure 1

- (d) Write an expression for small signal Hybrid model h parameters A_i , A_v , R_i , R_o for CE Voltage divider bias amplifier circuit with Emitter bypass capacitor (C_E).

SECTION-C

This Section consists of 5 theory questions. Each question is of 10 marks : $(10 \times 5 = 50)$

3. Attempt any **two** parts of the following : $(5 \times 2 = 10)$

- (a) Determine the current I as shown in Figure 2. Assume

Diode is silicon diode with $V_D = 0.7$ V :

 


Figure 2

- (b) Sketch output voltage (V_o) waveform of the following network as shown in Figure 3. Assume Diode is silicon diode with $V_D = 0.7$:

 


Figure 3

- (c) Calculate the current I_E , I_C and I_B for the following circuit as shown in Figure 4 :

 


Figure 4

4. Attempt any **two** parts of the following : $(5 \times 2 = 10)$

- (a) Draw the neat diagram structure of JFET and explain the transfer characteristic.
- (b) Explain Depletion type MOSFET with diagram and draw the transfer characteristics.
- (c) Show that the trans-conductance g_m of JFET is related to drain current I_{DS} by :

$$g_m = \frac{2}{V_P} \sqrt{I_{DSS} I_{DS}}$$

5. Attempt any **two** parts of the following : (5×2=10)

- Draw and explain the circuit diagram for performing the Differentiator operation using Op-Amp.
- Derive the output voltage (V_o) for the given Figure 5 :

 


Figure 5

- Find the output voltage (V_o) for the given circuit as shown in Figure 6 :

 


Figure 6

6. Attempt any **two** parts of the following : (5×2=10)

- Write De Morgan's and Duality theorem in Digital circuits.
 - Simplify the Complement of the logic function

$$F = ABC + ABC + \overline{ABC} + \overline{ABC}$$

- Simplify the following expression using K-map in Sum of Products (SOP) form.

$$F(A, B, C, D) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \sum d(0, 2, 14)$$

- Simplify the following expression using K-map in Product of Sum (POS) form :

$$F(A, B, C, D) = \prod M(0, 1, 3, 6, 7, 8, 9, 11, 13, 14, 15)$$

7. Attempt any **one** part of the following : (10×1=10)

- Using a suitable diagram explain the basic principle of a digital voltage meter.
- Describe the working of a CRO with the help of block diagram.
 - Explain the measurement of phase and frequency using CRO.